

EXPERIMENT No.: - 10

Simulation of VHDL Models.

TITLE:

Implementation of SR flip-flop in VHDL using Behavioural Modelling.

OBJECTIVE:

To implement the Behavioural model of SR flip-flop in ISE Simulator.

THEORY:

SR flip flop is one of the fundamental sequential circuit possible. This simple flip-flop is basically a one-bit memory storage device that has two inputs, one which will 'SET' the device (i.e., the output is 1), and is labelled S and other which will reset the device (i.e., the output is 0), labelled R. Thus, the name SR stands for "SET-RESET".


 


Fig.1 Symbol for SR flip flop

 

Since the SR flip-flop can be constructed by using clock transition, therefore we will provide a clock to SR flip-flop.

Thus, we can say

$$S^* = (S \cdot \text{CLOCK})' = S' \cdot \text{CLOCK}'$$

$$R^* = (R \cdot \text{CLOCK})' = R' \cdot \text{CLOCK}'$$

CASE 1: - Now if CLOCK is 0 then $S^*=1$ and $R^*=1$ and here S and R will be treated as don't care conditions, then we get Q and Q' in a memory state that is holding previous values.

CASE 2: - If CLOCK is 1 then $S^*=S'$ and $R^*=R'$, now there will be 4 more cases depending upon the values of S and R

- a.) $S=0$ and $R=0$ then S^* and R^* both becomes 1 and we get outputs Q and Q' holding memory state.
- b.) $S=0$ and $R=1$ then $S^*=1$ and $R^*=0$ then we get $Q=0$ and $Q'=1$, we get both outputs as complement of each other.
- c.) $S=1$ and $R=0$ then $S^*=0$ and $R^*=1$, then we get $Q=1$ and $Q'=0$.
- d.) $S=1$ and $R=1$ then $S^*=0$ and $R^*=0$ then we get Q and Q' in the invalid state, i.e., not used condition

The truth table of SR flip-flop is given below.

CLK	S	R	Q	\bar{Q}
0	×	×	Memory state	
1	0	0	Memory state	
1	0	1	0	1
1	1	0	1	0
1	1	1	Invalid	

SOURCE CODE: -

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity SR_flip_flop is
    Port ( S : in  STD_LOGIC;
          R : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          Q_bar : out STD_LOGIC;
          Q : out STD_LOGIC);
end SR_flip_flop;

architecture Behavioral of SR_flip_flop is
```

```


begin
    PROCESS(CLK)
        variable tmp: std_logic;
        begin
            if(CLK='1' and CLK' event) then
                if(S='0' and R='0')then
                    tmp:=tmp;
                elsif(S='1' and R='1')then
                    tmp:='Z';
                elsif(S='0' and R='1')then
                    tmp:='0';
                else
                    tmp:='1';
                end if;
            end if;
            Q <= tmp;
            Q_bar <= not tmp;
        end PROCESS;

end Behavioral;


```

OUTPUT: -


ENTITY DIAGRAM: -

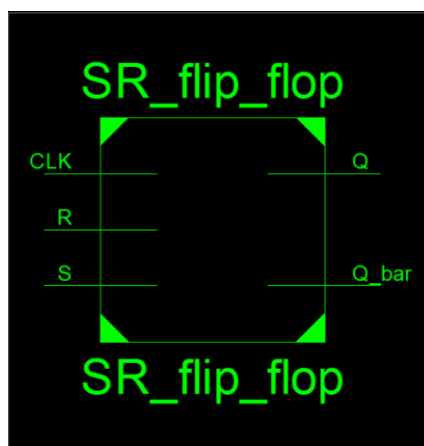

DETAILED ENTITY DIAGRAM: -

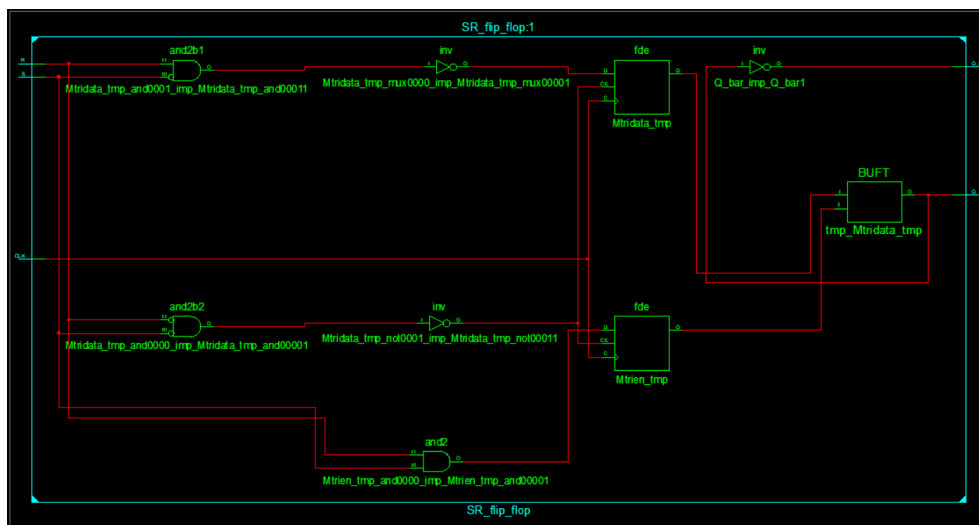

SIMULATION: -

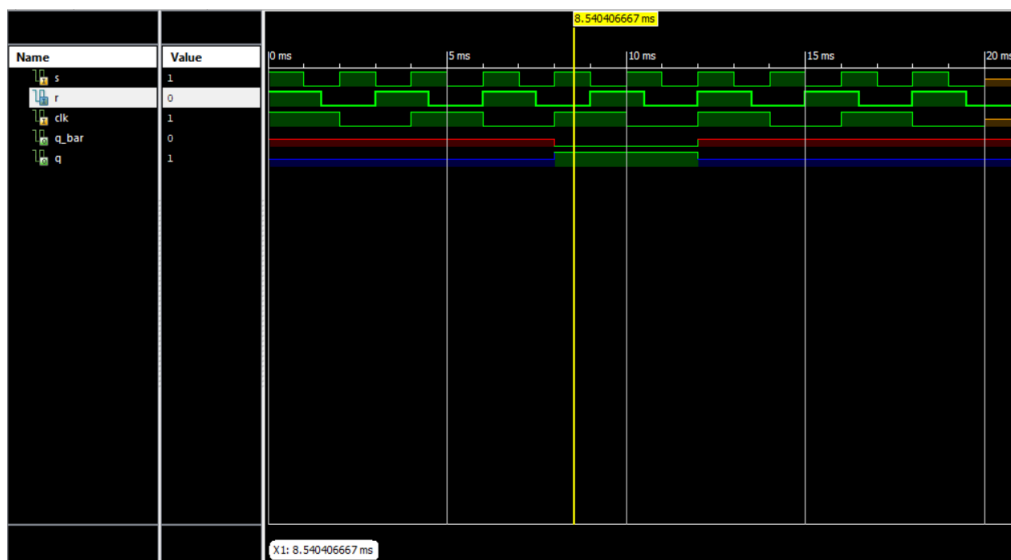

RESULT:

Thus, we have implemented the Behavioural Model of SR flip flop in VHDL, and the Entity Diagram and RTL are shown above. Also, the flip flop's truth table has been verified using the simulation of the waveform in ISE Simulator.

CONCLUSION:

In this experiment, we learnt about how to implement the Behavioural model of SR flip flop in VHDL and also verified the truth table of this flip flop using the waveform generated by ISE Simulator.