

EXPERIMENT No.: - 14

Simulation of VHDL Models.

TITLE:

Implementation of 8-bit Adder in VHDL using Structural Modelling.

OBJECTIVE:

To implement the Structural model of 8-bit Adder using ISE Simulator.

THEORY:

In an 8-bit adder the full adders are connected in a cascade with a 1 carry cascading from a least significant bit to the most significant bit. Complete 8-bit Adder: Technically the first Carry-In on the first full adder (also the full adder of the least significant bit) does not have to be there.

The truth table is as follows: -

Inputs			Output	
<i>A</i>	<i>B</i>	<i>C</i>	<i>C₁</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
1	0	0	0	1
0	1	1	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

SOURCE CODE: -

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;
```

entity bit8adder is

```
Port ( cin : in  STD_LOGIC;
      a0 : in  STD_LOGIC;
      a1 : in  STD_LOGIC;
      a2 : in  STD_LOGIC;
      a3 : in  STD_LOGIC;
      a4 : in  STD_LOGIC;
      a5 : in  STD_LOGIC;
      a6 : in  STD_LOGIC;
      a7 : in  STD_LOGIC;
      b0 : in  STD_LOGIC;
      b1 : in  STD_LOGIC;
      b2 : in  STD_LOGIC;
      b3 : in  STD_LOGIC;
      b4 : in  STD_LOGIC;
      b5 : in  STD_LOGIC;
      b6 : in  STD_LOGIC;
      b7 : in  STD_LOGIC;
      cout : out STD_LOGIC;
      s0 : out STD_LOGIC;
      s1 : out STD_LOGIC;
      s2 : out STD_LOGIC;
      s3 : out STD_LOGIC;
      s4 : out STD_LOGIC;
      s5 : out STD_LOGIC;
      s6 : out STD_LOGIC;
```

```

        s7 : out STD_LOGIC);
end bit8adder;

architecture structural of bit8adder is

    component FA is
        port(A, B, Cin : in std_logic;
              Cout, Sum: out std_logic);
    end component;


    signal c0, c1, c2, c3, c4, c5, c6: std_logic;
begin
    u1: FA port map(a0, b0, cin, c0, s0);
    u2: FA port map(a1, b1, c0, c1, s1);
    u3: FA port map(a2, b2, c1, c2, s2);
    u4: FA port map(a3, b3, c2, c3, s3);
    u5: FA port map(a4, b4, c3, c4, s4);
    u6: FA port map(a5, b5, c4, c5, s5);
    u7: FA port map(a6, b6, c5, c6, s6);
    u8: FA port map(a7, b7, c6, cout, s7);

end structural;

```

OUTPUT: -

DETAILED ENTITY DIAGRAM: -

 

RESULT:

Thus, through structural modelling we have implemented the 8-bit Adder in VHDL and we have processed the overview of the basic structure of this entity as a whole using the RTL schematics. The blank square correctly represents the structure of respective input, output Ports signals in Structural Modelling.

CONCLUSION:

In this experiment, we learnt about how to implement the 8-bit Adder in VHDL as the structural ports design and placement of the respective model's input and output is correctly represented using structural modelling.